

# Digital IC Design Training

---

Sep 25, 2018

Student: Jen-Hao Hsiao, Yu-Fen Wu

Professor: Wen-Long Chin



# Outline

---

- Finite State Machine
- Example: Bit-stream Pattern Detector

# Finite State Machine

---

What is FSM?

- A desired relationship between the input and the output sequences.
- FSM structures
  - Mealy machine
  - Moore machine

# Finite State Machine

---


- FSM structures

- Contains sequential networks and combinational logic.
- The sequential network is a set of flip-flops.
- Mealy machine: the output follows the **input and current state**.
- Moore machine: the output depends on the **current state only**.

# Finite State Machine

---

- FSM structures

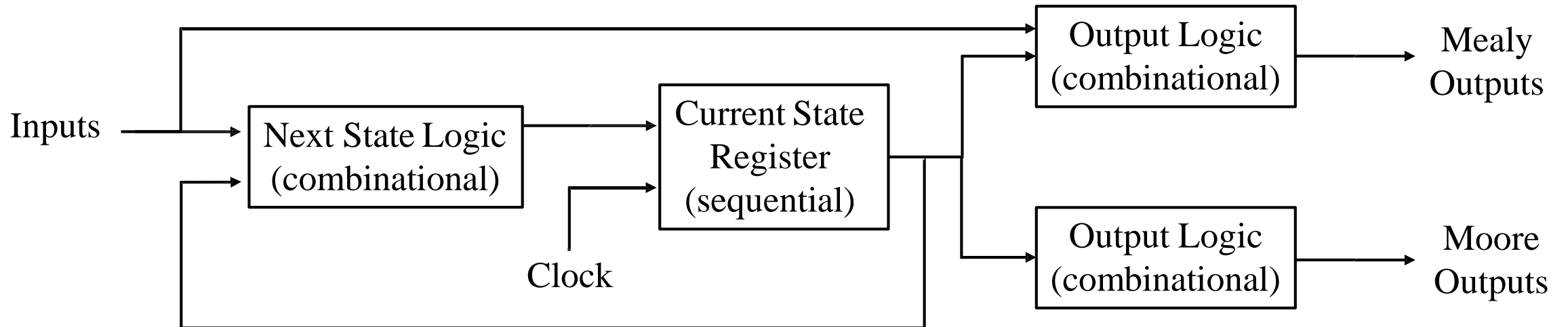


# Example: Bit-stream Pattern Detector

- Input 1-bit *bit\_in*. Output 1-bit *det\_out*.
- det\_out* gives 1 when *bit\_in* is 101.

*bit\_in* = 001011010110011  
*det\_out* = 000010010100000

Current State	Next state		Output (det_out)	
	<i>bit_in</i> =0	<i>bit_in</i> =1	<i>bit_in</i> =0	<i>bit_in</i> =1
S0	S0	S1	0	0
S1	S2	S1	0	0
S2	S0	S1	0	1

 


```

1  module fsm_bspd2(clk, reset, bit_in, det_out);
2  input clk, reset, bit_in;
3  output det_out;
4
5  reg [1:0] current_state;
6  reg [1:0] next_state;
7  wire det_out;
8
9  parameter    S0 = 2'b00,
10              S1 = 2'b01,
11              S2 = 2'b10;
12
13  //FSM current state register
14  always@(posedge clk or posedge reset)
15      if(reset==1)
16          current_state <= S0;
17      else
18          current_state <= next_state;
19

```

Current State	Next state		Output (det_out)	
	<i>bit_in=0</i>	<i>bit_in=1</i>	<i>bit_in=0</i>	<i>bit_in=1</i>
S0	S0	S1	0	0
S1	S2	S1	0	0
S2	S0	S1	0	1

 

Current State	Next state		Output (det_out)	
	<i>bit_in</i> =0	<i>bit_in</i> =1	<i>bit_in</i> =0	<i>bit_in</i> =1
S0	S0	S1	0	0
S1	S2	S1	0	0
S2	S0	S1	0	1

```

20 //FSM next state logic
21 always@(*)
22     case(current_state)
23     S0: next_state = (bit_in==1) ? S1 : S0;
24     S1: next_state = (bit_in==0) ? S2 : S1;
25     S2: next_state = (bit_in==1) ? S1 : S0;
26     default: next_state = S0;
27     endcase
28
29 //FSM output logic
30 assign det_out = ((current_state==S2) && (bit_in==1)) ? 1 : 0;
31
32 endmodule

```

