

NCKU-ES  
Digital IC Design

Lab1

Design of Multiplexers

Professor: Wen-Long Chin  
TA: Jen-Hao Hsiao, Yu-Fen Wu  
VLSI signal processing LAB

- Objectives

To familiarize with the basics of Verilog HDL

To learn the operations of Modelsim

- LAB contents

LAB1-1: 2-1 Mux

LAB1-2: 4-1 Mux


## LAB1-1: 2-1 Mux

### ● Design Description

A multiplexer (mux) is a device that chooses one of several input signals and forwards the selected input into a single line. A mux of  $2^n$  inputs has  $n$  select lines, which are used to choose which input line to send to the output.

Design a 2-1 mux by writing **Verilog structural code**

### ● Block Diagram

 

### ● Specifications

Top module name : mux\_2\_to\_1 (File name: mux\_2\_to\_1.v)

Input pins: a, b, sel

Output pins: M


All of the inputs and outputs are 1bit

## LAB1-2: 4-1 Mux

- Design Description

Please design a 4-1 mux by 2-1muxes you design in LAB1-1

- Block Diagram

 

- Specifications

Top module name : mux\_4\_to\_1 (File name: mux\_4\_to\_1.v)

Input pins: a, b, c, d, **sel[0:1]**

Output pins: M

## ● Note

須自行撰寫測試程式(Testbench)去驗證自己的作業

書面報告需包含

1. 設計原理(Design principle)
2. 邏輯閘(Gate level)架構
3. 波型(Waveform)分析

書面報告請勿手寫

繳交的作業資料夾組織與命名請與下頁圖示相同

作業繳交給人豪 jfslmarco@gmail.com

Due date: 2018/7/31(二)

- Directory Organization

