

NCKU-ES

Digital IC Design

Lab3

Bit-stream Pattern Detector

Professor: Wen-Long Chin
TA: Jen-Hao Hsiao, Yu-Fen Wu
VLSI signal processing LAB

- Objectives

To familiarize with RTL code


- LAB contents

LAB3: bit-stream pattern detector

● Design Description

- ◆ Please design a serial input bit-stream pattern detector module.
- ◆ Function : serial input bit-stream pattern detector. Using finite state Mealy-machine. “det_out” is to be low (logic0), unless the input bit-stream is “0010” sequentially. Example:
bit_in : 0 0 1 0 0 1 0 0 0 1 0 . . .
det_out : 0 0 0 1 0 0 1 0 0 0 1 0 . . .
- ◆ All inputs are synchronized at clock (clk) rising edge.
- ◆ It is synchronous reset architecture.

● Block Diagram

 

● Specifications

- ◆ Top module name : fsm_bspd (File name: fsm_bspd.v)
- ◆ Input pins : clk , reset , bit_in
- ◆ Output pins : det_out

- Note

本測驗提供測試程式(testbench)，各位同學之作業需能通過 testbench 的驗證，通過測試的截圖，如下

```
*****  
4013 Finish testing with no error  
*****
```